

9/2/2025

Single cycle RISC-V



Abd El Rahman Khaled Fouad Abd El Rahim

Table of contents

Abstract.....	3
Introduction.....	4
RISC-V Architecture.....	6
RISC-V instructions.....	9
Testing Script.....	11
Quest-Sim Snapshots.....	12
Elaborated Design Vivado.....	13
Schematic Design Vivado.....	14
Implementation Design Vivado.....	16
STA analysis and configurations.....	19
Udemy Certificate.....	21

Abstract

As shown In Figure 3.1, This project represents the design of RISC-V 32I microprocessor from scratch using HDL (Verilog) and tested using Questa-Sim by using exhausted testing of all possible different scenarios to maintain validation of all cases of the processor and implemented on Artix-7 (XC7A35TICPG236-1L) FPGA on Vivado by using a 12ns clock to solve any timing violations

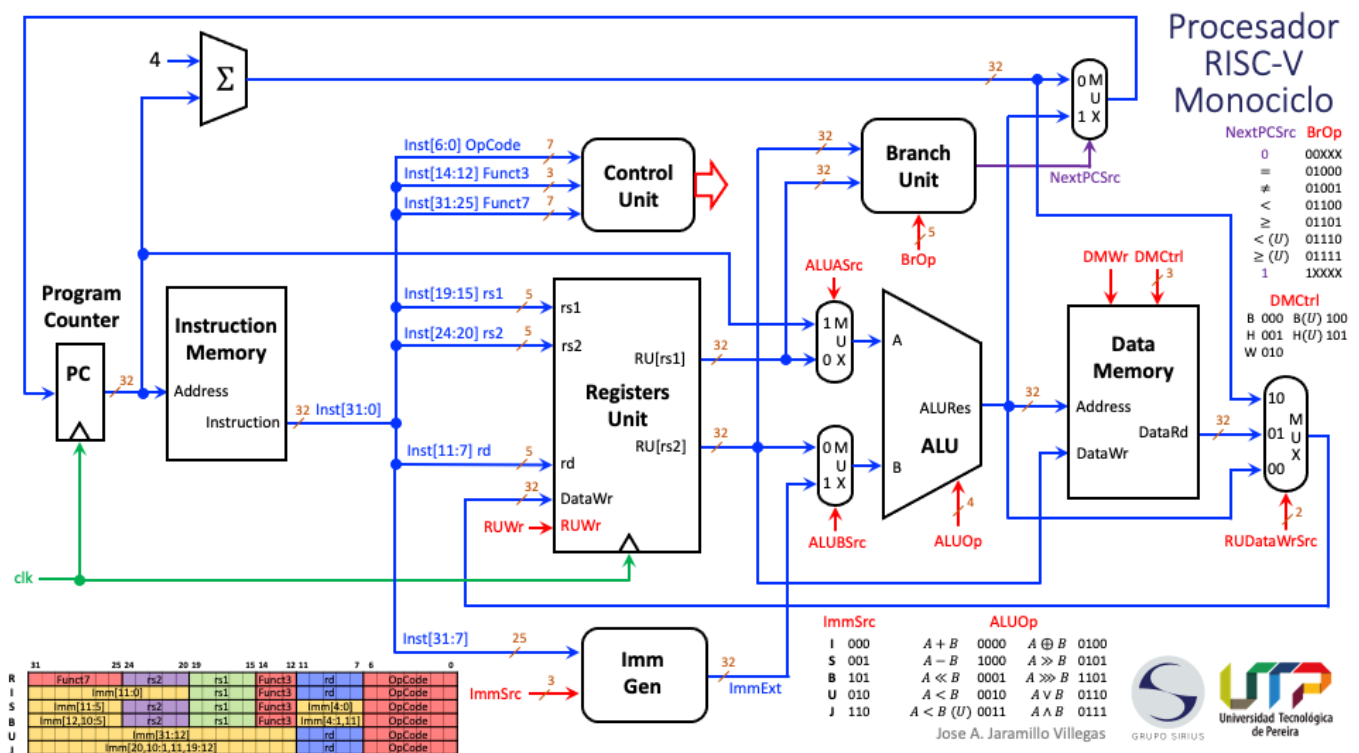


Figure 3.1 Single cycle RISC-V processor

Introduction

RISC-V (Reduced Instruction Set Computing - Version Five) is an open-source and highly flexible instruction set architecture (ISA) that has gained significant traction in recent years. Unlike proprietary architectures such as ARM or x86, RISC-V is free to use and allows for customization, making it a preferred choice for a wide range of applications.

The RISC-V ISA follows the RISC (Reduced Instruction Set Computing) principles, which emphasize simplicity, efficiency, and modularity. It provides a base integer instruction set (RV32I, RV64I, RV128I) and various optional extensions (such as floating-point, vector processing, and atomic operations), making it suitable for different computing needs.

That processor has different Applications in the industry: -

- Embedded Systems:
 - 1) Used in IoT devices, microcontrollers, and sensors.
 - 2) Low power consumption makes it ideal for battery-powered applications.
- Artificial Intelligence & Machine Learning:
 - 1) Custom RISC-V cores optimize **AI and deep learning** workloads.
 - 2) Used in AI accelerators and edge computing devices.
- High-Performance Computing (HPC):
 - 1) RISC-V is being explored for **supercomputers** and **data centers**.
 - 2) Efficient vector processing extensions enhance performance in **scientific computing**.

- Consumer Electronics:
 - 1) Found in **smartphones, wearables, and smart TVs.**
 - 2) Companies like **Google, Western Digital, and NVIDIA** have shown interest in RISC-V-based designs.

- Education & Research
 - 1) Open-source nature makes RISC-V popular in **universities and research labs.**
 - 2) Used for teaching computer architecture and experimenting with custom instruction sets.

RISC-V architecture

Any microprocessor hardware contains the following: -

- **Fetch:** get the instruction from instruction memory
- **Decode:** understand what this instruction does
- **Execute:** get the data needed to perform the operation and do the operation indicated in the instruction
- **Mem op:** some instructions require data memory access such as (load & store)
- **Write back:** write the results in the registers (internal to processor)
- memory operation

 


Figure 6.1

In Figure 7.1 represents the instruction memory, register file, and data memory are all read combinatorially. In other words, if the address changes, then the new data appears at RD after some propagation delay; no clock is involved. The clock controls writing only. These memories are written only on the rising edge of the clock. In this fashion, the state of the system is changed only at the clock edge. The address, data, and write enable must set up before the clock edge and must remain stable until a hold time after the clock edge. Because the state elements change their state only on the rising edge of the clock, they are synchronous sequential circuits. A microprocessor is built of clocked state elements and combinational logic, so it too is a synchronous sequential circuit. Indeed, a processor can be viewed as a giant finite state machine or as a collection of simpler interacting state machines.

 


Figure 7.1 State elements of a RISC-V processor

In Figure 7.2 the extend unit at which the processor adds the base address to the offset to find the address to read from memory.

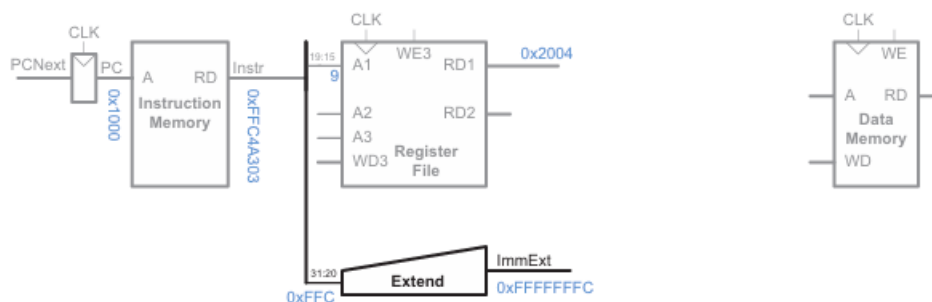


Figure 7.2 Extend unit

In Figure 8.1 shows the complete single cycle processor after putting the control unit that controls all the signals in the processor

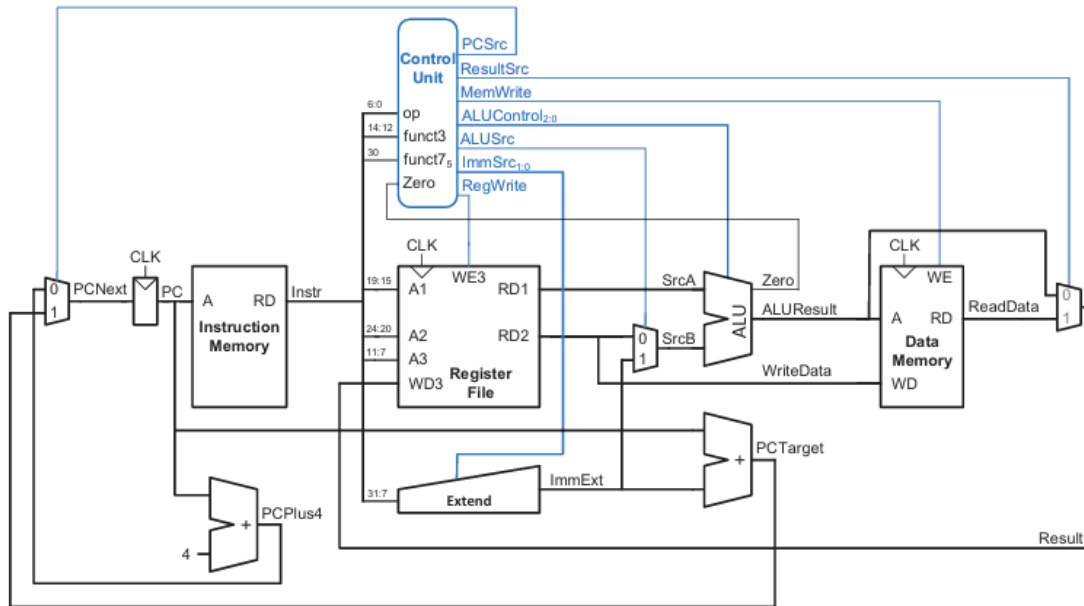


Figure 8.1 Complete single cycle processor

RISC-V instructions

- **Base Integer Instruction Set (I)**
 - Load and Store Instructions (LW, SW...)
 - Arithmetic Instructions (ADD, ADDI...)
 - Logical Instructions (AND, OR XOR...)
 - Comparison Instructions (SLT, SLTI...)
 - Branch Instructions (Conditional Jumps) (BEQ, BGE...)
 - Jump Instructions (Unconditional Jumps) (JAL, JALR...)
- **Multiplication and Division Extension (M)**
- **Atomic Extension (A)**
- **Floating-Point Extensions (F and D)**
- **Compressed Instructions (C)**
- **Vector Extension (V)**
- **Bit Manipulation Extension (B)**

But in my design, I will be focusing on the Base Integer Instruction Set (I) as shown in Figure 10.1

Appendix B. RISC-V Instruction Set Summary

31:25	24:20	19:15	14:12	11:7	6:0	
func7	rs2	rs1	func3	rd	op	R-Type
imm _{11:0}		rs1	func3	rd	op	I-Type
imm _{11:5}	rs2	rs1	func3	imm _{4:0}	op	S-Type
imm _{12:10,5}	rs2	rs1	func3	imm _{4:1,11}	op	B-Type
imm ₁₂				rd	op	U-Type
imm _{10,10,11,10,10}				rd	op	J-Type
fs3	func2	fs2	fs1	func3	fd	R4-Type
5 bits	2 bits	5 bits	5 bits	3 bits	5 bits	7 bits

Figure 8.1 RISC-V 32-bit instruction formats

- imm: signed immediate in imm_{11:0}
- uimm: 5-bit unsigned immediate in imm_{4:0}
- upimm: 20 upper bits of a 32-bit immediate, in imm_{20:12}
- Address: memory address: rs1 + SignExt(imm_{11:0})
- [Address]: data at memory location Address
- BTA: branch target address: PC + SignExt(imm_{12:10,1'b0})
- JTA: jump target address: PC + SignExt(imm_{12:10,1'b0})
- label: text indicating instruction address
- SignExt: value sign-extended to 32 bits
- ZeroExt: value zero-extended to 32 bits
- CSP: control and status register

Table B.1 RV32I: RISC-V integer instructions

op	func3	func7	Type	Instruction	Description	Operation
0000011 (3)	000	-	I	lb rd, imm(rs1)	load byte	rd = SignExt([Address] _{7:0})
0000011 (3)	001	-	I	lh rd, imm(rs1)	load half	rd = SignExt([Address] _{15:0})
0000011 (3)	010	-	I	lw rd, imm(rs1)	load word	rd = [Address] _{31:0}
0000011 (3)	100	-	I	lbu rd, imm(rs1)	load byte unsigned	rd = ZeroExt([Address] _{7:0})
0000011 (3)	101	-	I	lhu rd, imm(rs1)	load half unsigned	rd = ZeroExt([Address] _{15:0})
0010011 (19)	000	-	I	addi rd, rs1, imm	add immediate	rd = rs1 + SignExt(imm)
0010011 (19)	001	0000000*	I	slli rd, rs1, uimm	shift left logical immediate	rd = rs1 << uimm
0010011 (19)	010	-	I	slti rd, rs1, imm	set less than immediate	rd = (rs1 < SignExt(imm))
0010011 (19)	011	-	I	sltiu rd, rs1, imm	set less than imm. unsigned	rd = (rs1 < SignExt(imm))
0010011 (19)	100	-	I	xori rd, rs1, imm	xor immediate	rd = rs1 ^ SignExt(imm)
0010011 (19)	101	0000000*	I	srlr rd, rs1, uimm	shift right logical immediate	rd = rs1 >> uimm
0010011 (19)	101	0100000*	I	srair rd, rs1, uimm	shift right arithmetic imm.	rd = rs1 >>> uimm
0010011 (19)	110	-	I	ori rd, rs1, imm	or immediate	rd = rs1 SignExt(imm)
0010011 (19)	111	-	I	andir rd, rs1, imm	and immediate	rd = rs1 & SignExt(imm)
0010111 (23)	-	-	U	auipc rd, upimm	add upper immediate to PC	rd = (upimm, 12'b0) + PC
0100011 (35)	000	-	S	sb rs2, imm(rs1)	store byte	[Address] _{7:0} = rs2 _{7:0}
0100011 (35)	001	-	S	sh rs2, imm(rs1)	store half	[Address] _{15:0} = rs2 _{15:0}
0100011 (35)	010	-	S	sw rs2, imm(rs1)	store word	[Address] _{31:0} = rs2
0110011 (51)	000	0000000	R	add rd, rs1, rs2	add	rd = rs1 + rs2
0110011 (51)	000	0100000	R	sub rd, rs1, rs2	sub	rd = rs1 - rs2
0110011 (51)	001	0000000	R	sll rd, rs1, rs2	shift left logical	rd = rs1 << rs2 _{4:0}
0110011 (51)	010	0000000	R	slt rd, rs1, rs2	set less than	rd = (rs1 < rs2)
0110011 (51)	011	0000000	R	sltu rd, rs1, rs2	set less than unsigned	rd = (rs1 < rs2)
0110011 (51)	100	0000000	R	xor rd, rs1, rs2	xor	rd = rs1 ^ rs2
0110011 (51)	101	0000000	R	srl rd, rs1, rs2	shift right logical	rd = rs1 >> rs2 _{4:0}
0110011 (51)	101	0100000	R	sra rd, rs1, rs2	shift right arithmetic	rd = rs1 >>> rs2 _{4:0}
0110011 (51)	110	0000000	R	or rd, rs1, rs2	or	rd = rs1 rs2
0110011 (51)	111	0000000	R	and rd, rs1, rs2	and	rd = rs1 & rs2
0110111 (55)	-	-	U	lui rd, upimm	load upper immediate	rd = (upimm, 12'b0)
1100011 (99)	000	-	B	beq rs1, rs2, label	branch if =	if (rs1 == rs2) PC = BTA
1100011 (99)	001	-	B	bne rs1, rs2, label	branch if ≠	if (rs1 ≠ rs2) PC = BTA
1100011 (99)	100	-	B	blt rs1, rs2, label	branch if <	if (rs1 < rs2) PC = BTA
1100011 (99)	101	-	B	bge rs1, rs2, label	branch if ≥	if (rs1 ≥ rs2) PC = BTA
1100011 (99)	110	-	B	bltu rs1, rs2, label	branch if < unsigned	if (rs1 < rs2) PC = BTA
1100011 (99)	111	-	B	bgeu rs1, rs2, label	branch if ≥ unsigned	if (rs1 ≥ rs2) PC = BTA
1101111 (103)	000	-	J	jalr rd, rs1, imm	jump and link register	PC = rs1 + SignExt(imm), rd = PC + 4
1101111 (111)	-	-	J	jal rd, label	jump and link	PC = JTA, rd = PC + 4

*encoded in instr_{7:25}, the upper seven bits of the immediate field

Figure 10.1

Testing script

I validate the design functionality by exhausted testing script that tests all the instructions as shown in Figure 11.1 and if in address 100 (25 in hexadecimal) value =25 then the design functionality is successfully completed

```
# riscvtest.s
# Sarah.Harris@unlv.edu
# David_Harris@hmc.edu
# 27 Oct 2020
#
# Test the RISC-V processor:
#   add, sub, and, or, slt, addi, lw, sw, beq, jal
# If successful, it should write the value 25 to address 100
#
# RISC-V Assembly      Description      Address  Machine Code
main:  addi x2, x0, 5      # x2 = 5          0         00500113
      addi x3, x0, 12     # x3 = 12         4         00C00193
      addi x7, x3, -9     # x7 = (12 - 9) = 3  8         FF718393
      or   x4, x7, x2     # x4 = (3 OR 5) = 7  C         0023E233
      and  x5, x3, x4     # x5 = (12 AND 7) = 4 10        0041F2B3
      add  x5, x5, x4     # x5 = 4 + 7 = 11   14        004282B3
      beq  x5, x7, end    # shouldn't be taken 18        02728863
      slt  x4, x3, x4     # x4 = (12 < 7) = 0  1C        0041A233
      beq  x4, x0, around # should be taken   20        00020463
      addi x5, x0, 0     # shouldn't execute  24        00000293
around: slt  x4, x7, x2   # x4 = (3 < 5) = 1   28        0023A233
      add  x7, x4, x5     # x7 = (1 + 11) = 12 2C        005203B3
      sub  x7, x7, x2     # x7 = (12 - 5) = 7  30        402383B3
      sw   x7, 84(x3)     # [96] = 7         34        0471AA23
      lw   x2, 96(x0)     # x2 = [96] = 7     38        06002103
      add  x9, x2, x5     # x9 = (7 + 11) = 18 3C        005104B3
      jal  x3, end        # jump to end, x3 = 0x44 40       008001EF
      addi x2, x0, 1     # shouldn't execute  44        00100113
end:    add  x2, x2, x9    # x2 = (7 + 18) = 25 48        00910133
      sw   x2, 0x20(x3)   # [100] = 25       4C        0221A023
done:   beq  x2, x2, done  # infinite loop     50        00210063
```

Figure 11.1 Testing script

Quest-Sim Snapshots

In Figure 12.1 the result of my testing script will be shown in Address number 100 (25 in hexadecimal) and the design functionality is successfully completed

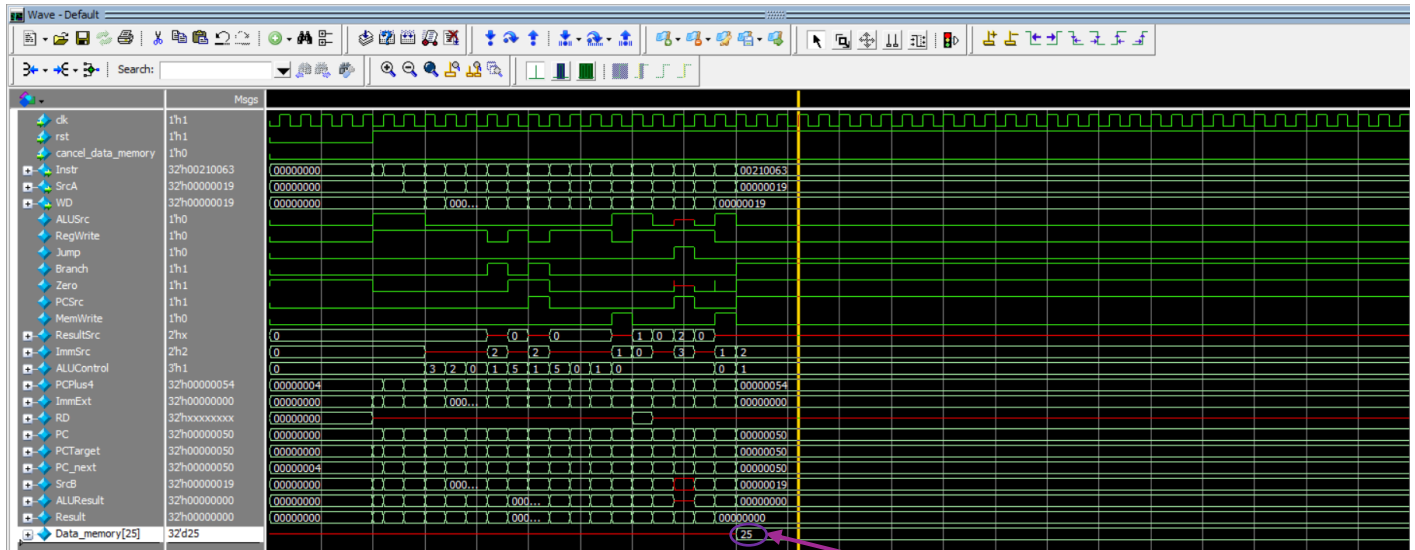


Figure 12.1 Questa-Sim snapshots

Elaborated Design Vivado

I used Artix-7 (XC7A35TICPG236-1L) FPGA on Vivado by using a 12 ns clock for my design and the elaborated design in Figure 13.1

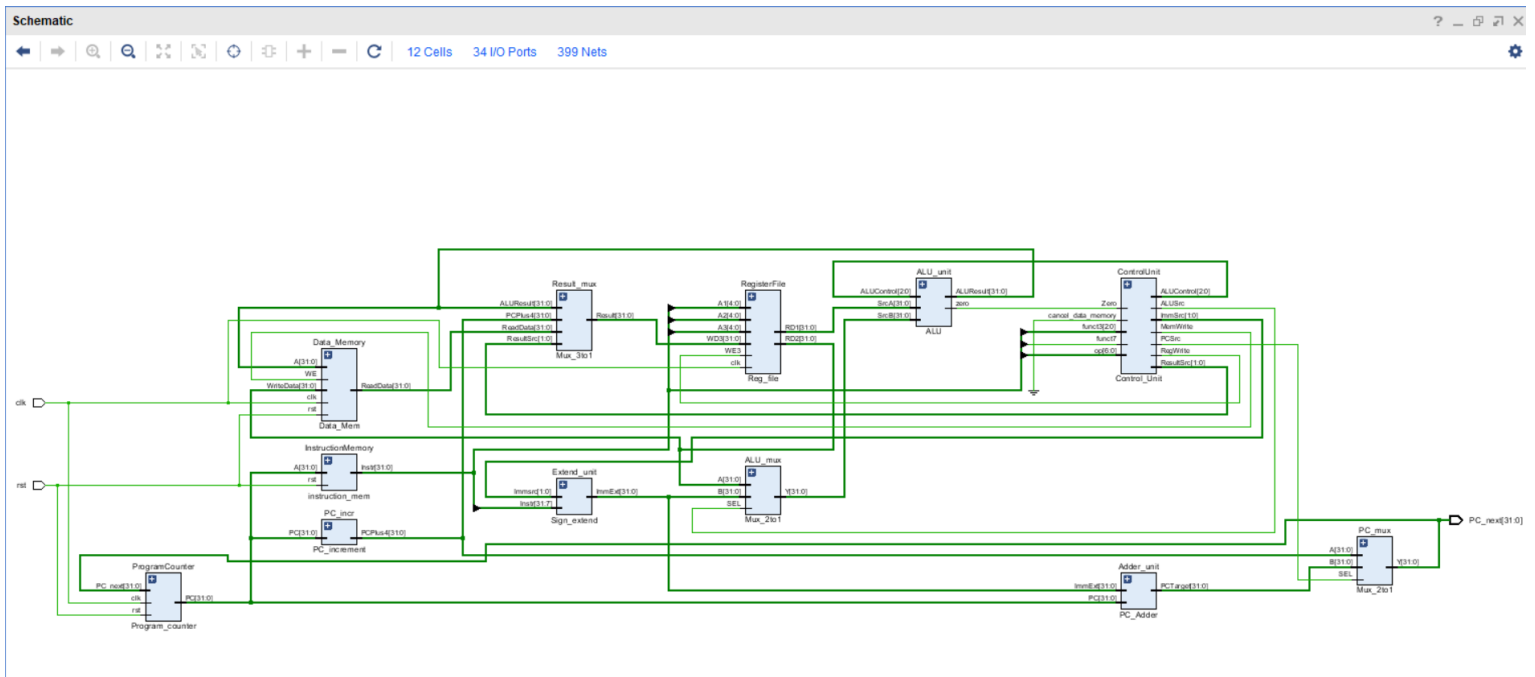


Figure 13.1 Elaborated Design

In Figure 13.2, the messages of the report of the elaborated design showing there are no errors



Figure 13.2

Schematic Design Vivado

Now let's move forward to the next step which is synthesizing the design and Figures 14.1 and 15.1 shows the schematic of the synthesized design

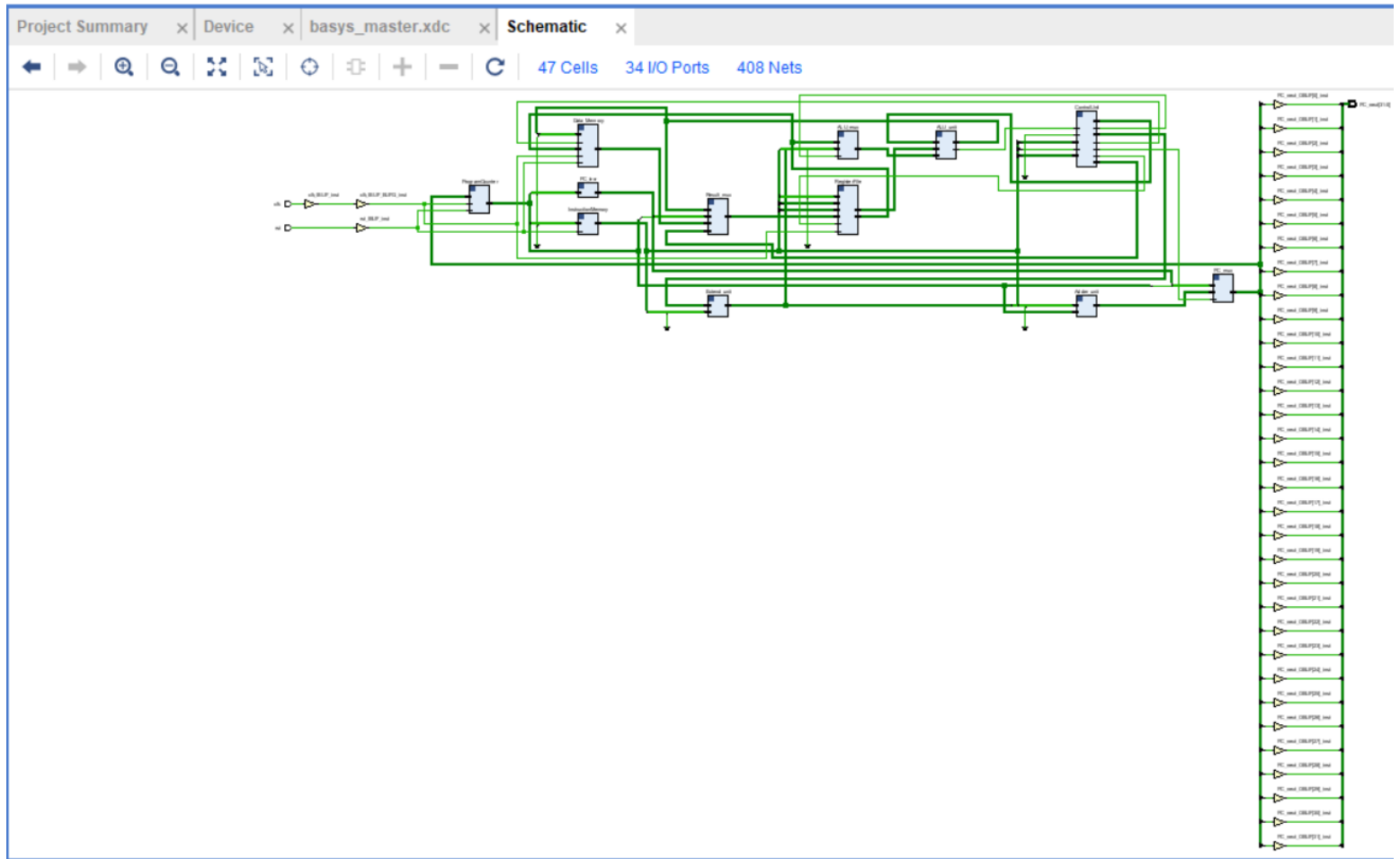


Figure 14.1 overall synthesized design

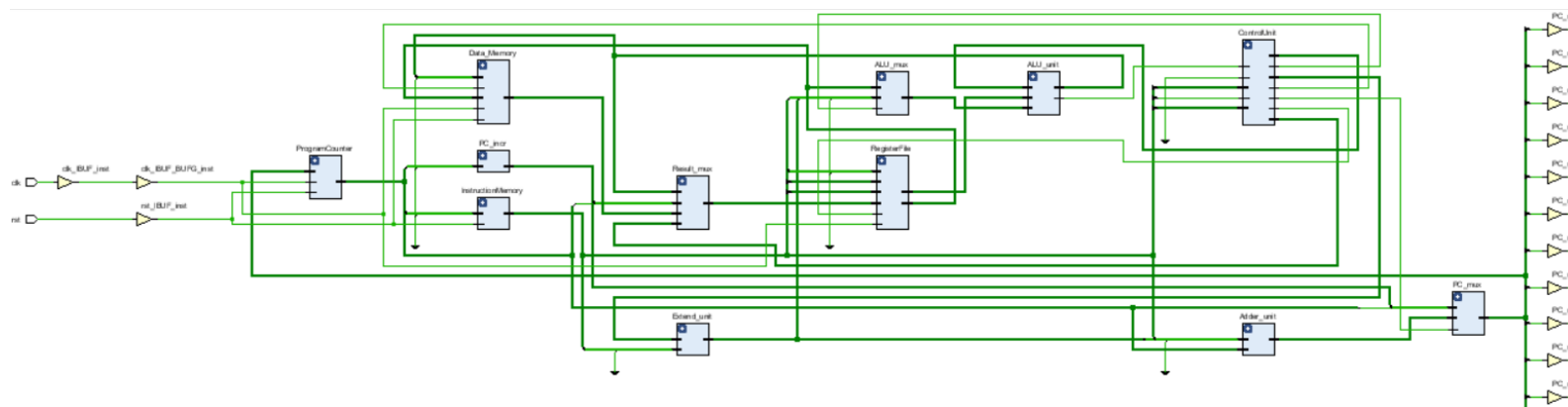


Figure 15.1 Zoomed in Synthesized design

In Figures 15.2 and 15.3 shows that there are no errors in the synthesized design, and it is done successfully

 


Figure 15.2 Messages of synthesized design

 


Figure 15.3 Methodology of synthesized design

Implementation Design Vivado

As we completed the synthesization of the design let's move forward to the implementation step as shown in Figure 16.1

 


Figure 16.1 Implementation Design

In Figures 17.1 and 17.2 show that there are no errors in the implemented design, and it is done successfully

 


Figure 17.1 Message of implemented design

 


Figure 17.2 Methodology of implemented design

In Figure 17.3 shows the utilization of the implemented design on the FPGA used (Artix-7)

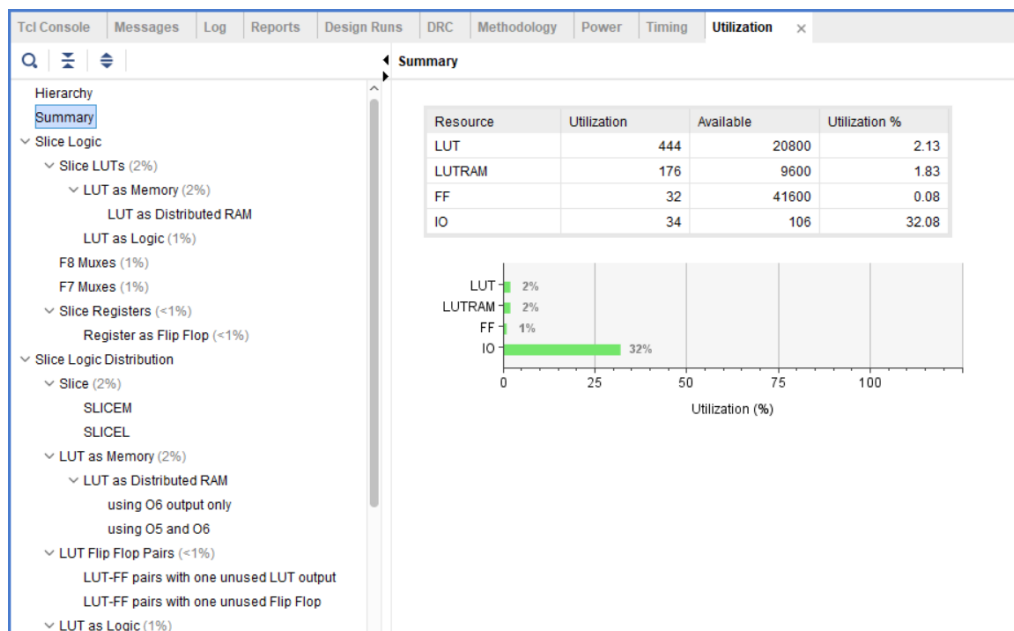


Figure 17.3 Utilization report of the implemented design

In Figure 18.1 clarifies the Power report of the implementation and shows the static power and dynamic power of the design

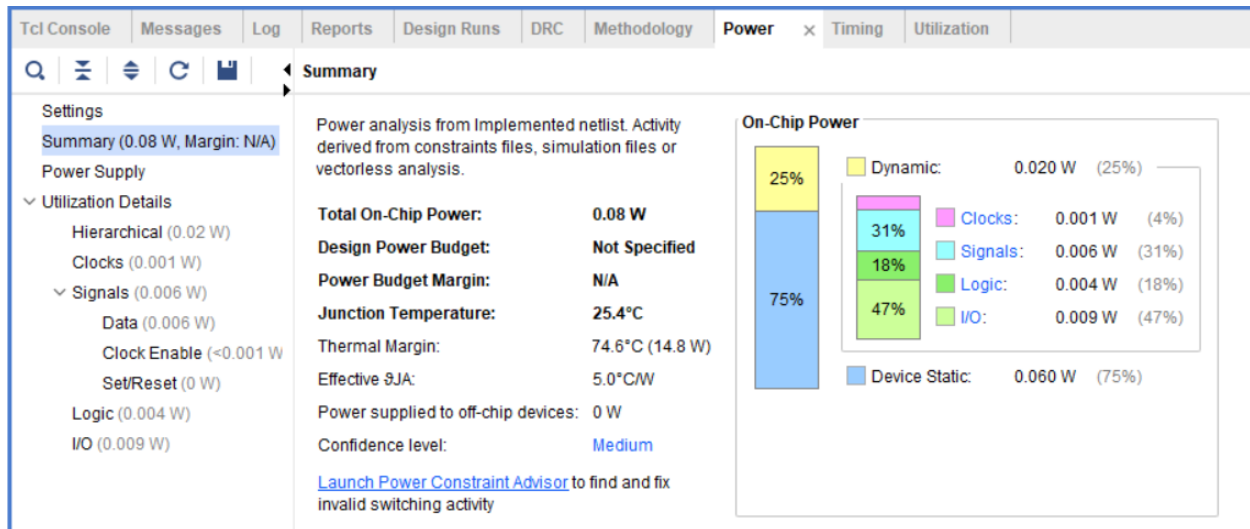


Figure 18.1 Power report of the implemented design

STA analysis and configurations

RISC-V is designed with 12 ns clock to solve any time violations such as hold time violations and setup time violations, and we will take a closer look at the lowest delay path that is related to the hold time and most delay path (critical path) that is related to the setup time and make sure that our design is clear of violations.

In Figure 19.1 shows the Critical path of the implemented design and in Figure 19.2 shows the lowest delay path of the design

 


Figure 19.1 Critical path

 


Figure 19.2 lowest delay path

In Figure 20.1 the timing report of the implemented design is clear of any violations as the slack is a positive value

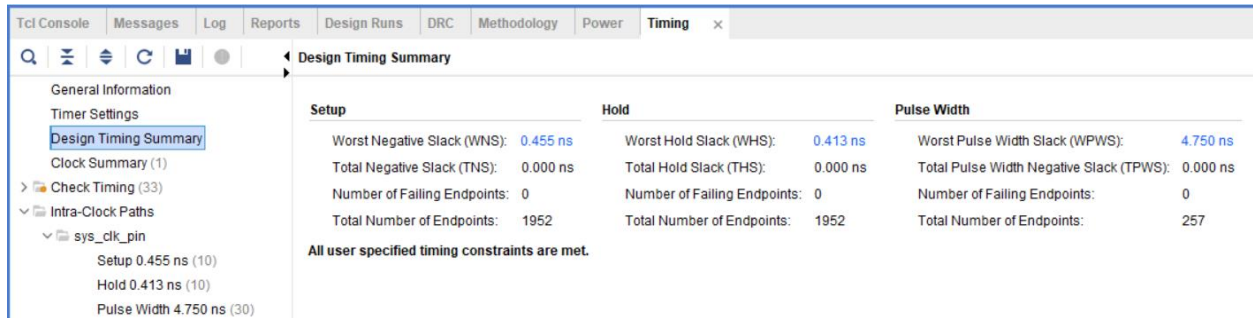


Figure 20.1 Timing report of the implemented design

Udemy Certificate



Certificate no: UC-67b30795-775a-4d7b-9fd3-0a5c4e8bda0
Certificate url: ude.my/UC-67b30795-775a-4d7b-9fd3-0a5c4e8bda0
Reference Number: 0004

CERTIFICATE OF COMPLETION

Building a RISC-V SoC From Scratch!

Instructors **Mohamed Nasser, Abdulaziz El-Safty, Ramy Rabie**

Abdelrahman Khaled Fouad Abdelrahim

Date **Feb. 9, 2025**

Length **6.5 total hours**